

Assigned-1

Sachin V
RARE1100410000
ECE A

Analog and linear equation

1) input independence $\Rightarrow \frac{5-0.7}{180k\Omega} = 0.0238 \mu$

$$V_{CE} = V_{CC} - I_C R_L$$
$$= 9 - 0.0238 \cdot 32 = 0.1$$

2)

a) Transistor parameter

$$100 \cdot V_A = 100$$

to calculate small signal parameters for each transistor we need 1 PNP

$$V_O = g_m V_A (V_{O1} \parallel R_L)$$

$$V_n = -V_C \cdot g_m$$

$$\frac{R_S \parallel R_n}{R_S \parallel R_n} \cdot \frac{A_V = V_O}{V_S} = \frac{(g_m V_n) (R_{O1} \parallel R_C)}{\gamma B + \gamma n}$$

$$= -\frac{B}{128 + V_n}$$

b) $g_m, \gamma n, \gamma B$

$g_m = I_C / V_T$ for each transistor

$$\gamma n = \frac{B}{g_m} \text{ do is output resistance}$$

$$g_m = \frac{V_O}{V_n} \quad || R_{O1} || R_C$$

c) Small signal voltage gain A_{V1}

$$A_{V1} = -g_m \text{ for the transistor current to } V_{O1}$$

d) Small signal voltage gain A_{V2}

$$A_{V2} = -g_m R_T \text{ for transistor between}$$

c) Overall small signal voltage gain A_V

$$A_V = A_{V1} \times A_{V2}$$

3)

a) To calculate voltage across speaker using power and resistance relation S_p

$$P = \frac{V^2}{R} = \frac{24^2}{10.8} = \frac{576}{2} = 288 \text{ watt}$$

b) To select transistor type and biasing

* choose and appropriate transistor based on application

* determine the biasing condition for the transistor

c) calculate the collector current (I_C)

$$I_C \approx I_B / \beta \text{ where } I_B \text{ is base current through speaker}$$

$$d) \cdot R_C = \frac{V_C}{I_C} = \frac{24}{\frac{100}{20}} = 5$$

e) power rectifying

$$P_C = I_C^2 \times R_C \text{ where transistor can be handle the collector current and power}$$

$$P_C = I_C^2 \times R_C = 0.3 \times 10^2 = 30 \text{ watt}$$

$$A_v = \left(\frac{R_C R_C}{R_E} \right)$$

linear that $\beta = 125$, $R_C = 4 \text{ k}\Omega$, $R_E = 3 \text{ k}\Omega$

$$A_v = 125 \times \frac{4}{3} = 41.6 \times 4$$

$$= 166.4$$

~~$$A_v = 125 \times \frac{4}{3} = 166.4$$~~

$$A_v = \frac{V_{CC} - I_C R_C}{R_C}$$

$$= \frac{134 - 3}{10} = 0.96 \text{ Voltage gain}$$

Tubuh