

## Case Study - 1

## Analog & Linear Electronic Circuits

i) Discuss the working

Series Regulator fixed voltage Series Regulator

→ It is a type of voltage regulator that maintains a constant o/p voltage regulator a change in i/p voltage or load condition.

(i) Block Diagram

It consist of a Series pass transistor voltage reference feedback network and control circuit

ii) Voltage reference,

It provide a stable reference voltage against which the o/p voltage is compared the reference voltage is typically derived from a Zener diode or bandgap reference circuit

iii) feedback network

It compare the o/p voltage against the reference voltage Operator error signal based on diff b/w 2 voltage

iv) Series pass transistor

It acts as a variable section b/w the i/p o/p terminate by adjust the reference resistance the voltage is regulated to the load the transistor excess power as heat when the voltage



## Carrier frequency generation:

The PLL generates a stable and accurate carrier frequency typically in the audio frequency range which serves as the basis for the synthesized sound.

## ii) Frequency modulation

The O/P of PLL serves as the carrier signal while the audio signal acts as the modulating signal. The frequency of the carrier signal is modulated by the instantaneous amplitude of the audio signal, resulting in a change in pitch of the note.

## iii) Complex waveform modulation

By modulating the carrier frequency with various audio signals including single notes or more complex sounds, a wide range of sounds can be synthesized from traditional musical instruments to abstract electronic textures.

## Time in FM synthesis:

Time plays a crucial role in FM synthesis by controlling the timing of detection of various levels within the synthesis process.



is high than the o/p voltage

v) regulation

The regulator also compensates for change in i/p voltage to maintain a constant o/p voltage. This ensures stable operation even when the i/p voltage fluctuates. Overall, the fixed voltage series regulator provides a  $\approx 6\%$  reliable of stable o/p voltage. Series regulators provide a  $\approx 6\%$  reliable of stable o/p voltage, making it suitable for various applications where precise voltage regulation provides a variable voltage power supply for electronic device voltage reference voltage stability.

- x Explain the working IC 723 general purpose regulator the  $\approx$  and the operation o/p voltage.
- The IC 723 is popular general purpose voltage generator IC that can be configured to provide both positive and the regulated voltage.

working principle

1) Reference Voltage

It uses a stable voltage reference circuit to generate a provide reference voltage to the IC 723 for the regulator configuration.



(ii)

### Feedback network

A feedback network is employed provide in prior the regulation transient response it consist of resistor of capacitor to control the loop gain bandwidth of regulator

Exp for output voltage ( $V_{out}$ ):

$$V_{out} = V_{ref} \times \left( 1 + \frac{R_2}{R_1} \right) + I_{adj} \times R_2$$

voltage gain (AV):

$$AV = \frac{V_{out}}{V_{ref}} = \frac{R_2}{R_1}$$

IC 723 provides a flexi and reliable solution for voltage regulation in various electronic units with o/p voltage gain easily adjustable by selecting appropriate resistor values in feedback network

(5)

Discuss any one application of phase lock timer

Phase locked loop (PLL) timer

One application that leverage the both phase locked loop (PLS) 2 times is frequency modulation m } Synthesis in electronic music production.

Phase-locked loop (PLL) in FM Synthesis

in fm Synthesis a pll can be used to generate peak carrier frequency that are modulated by an audio signal to create complex a dynamic sound

22/3